

# Assignment 2

IT<sub>451</sub> : COA LAB

**SOUMABRATA  
BHATTACHARYA**

IT, 4<sup>th</sup> Semester  
ID: 510817021 (Hx-20)

11-03-2019

## Question 1

Design and simulate the behavioral model of an UP/DOWN counter that is capable of counting up to 10. Use one input `count_mode` to control the mode of counting i.e. for `count_mode = '1'` the counter will operate as an UP counter and for `count_mode = '0'` the counter will behave as a DOWN counter. Use a reset input to reset the counter anytime to 0.

- Simulate and record the waveform with all possible stimulus waveforms.
- Synthesize the above circuit for Spartan 3 AN Evaluation Board. Observe and report the hardware utilization with the detailed schematics (both RTL and Technical).
- Synthesize the same design for Spartan 6 and compare the hardware utilization summary.

### VHDL Module:     *mod\_Counter.vhd*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity mod_Counter is
    Port ( clk          : in  STD_LOGIC;
          reset         : in  STD_LOGIC;
          count_mode     : in  STD_LOGIC;
          value          : out STD_LOGIC_VECTOR (3 downto 0));
end mod_Counter;

architecture Behavioral of mod_Counter is
    signal c : STD_LOGIC_VECTOR (3 downto 0);
begin

    process(clk, count_mode)
    begin
        if (reset = '1') then c <= "0000";
        elsif rising_edge(clk) then
            if(count_mode = '1') then
                if (c /= "1001") then
                    c <= std_logic_vector(unsigned(c) + 1);
                else c <= std_logic_vector(unsigned(c) + 7);
                end if;
            else
                if (c /= "0000") then
                    c <= std_logic_vector(unsigned(c) - 1);
                else c <= std_logic_vector(unsigned(c) + 9);
                end if;
            end if;
        end if;
    end process;
end;
```

```

end process;
    value <= c;

```


```

end Behavioral;


```

## SPARTAN 3AN

### RTL Schematic:

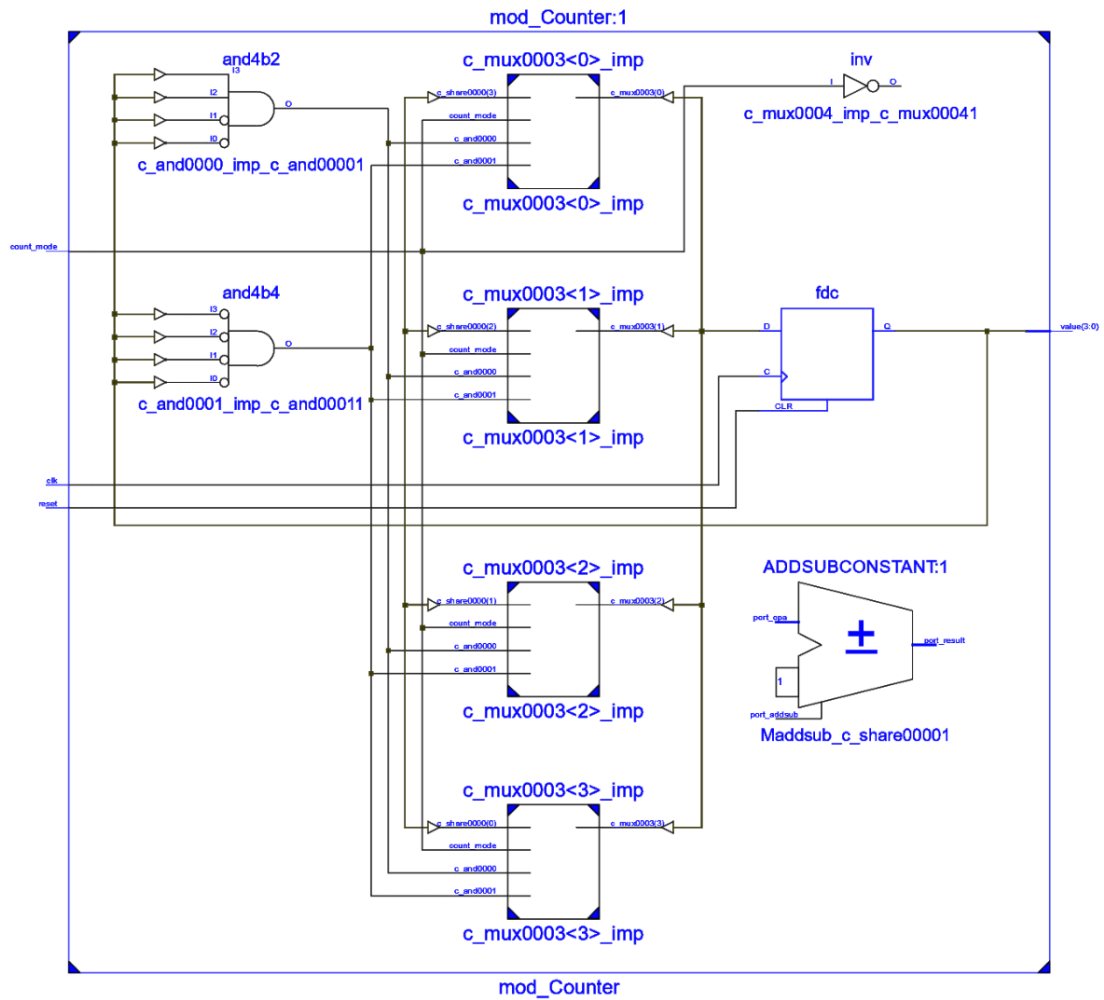

## Technology Schematic:

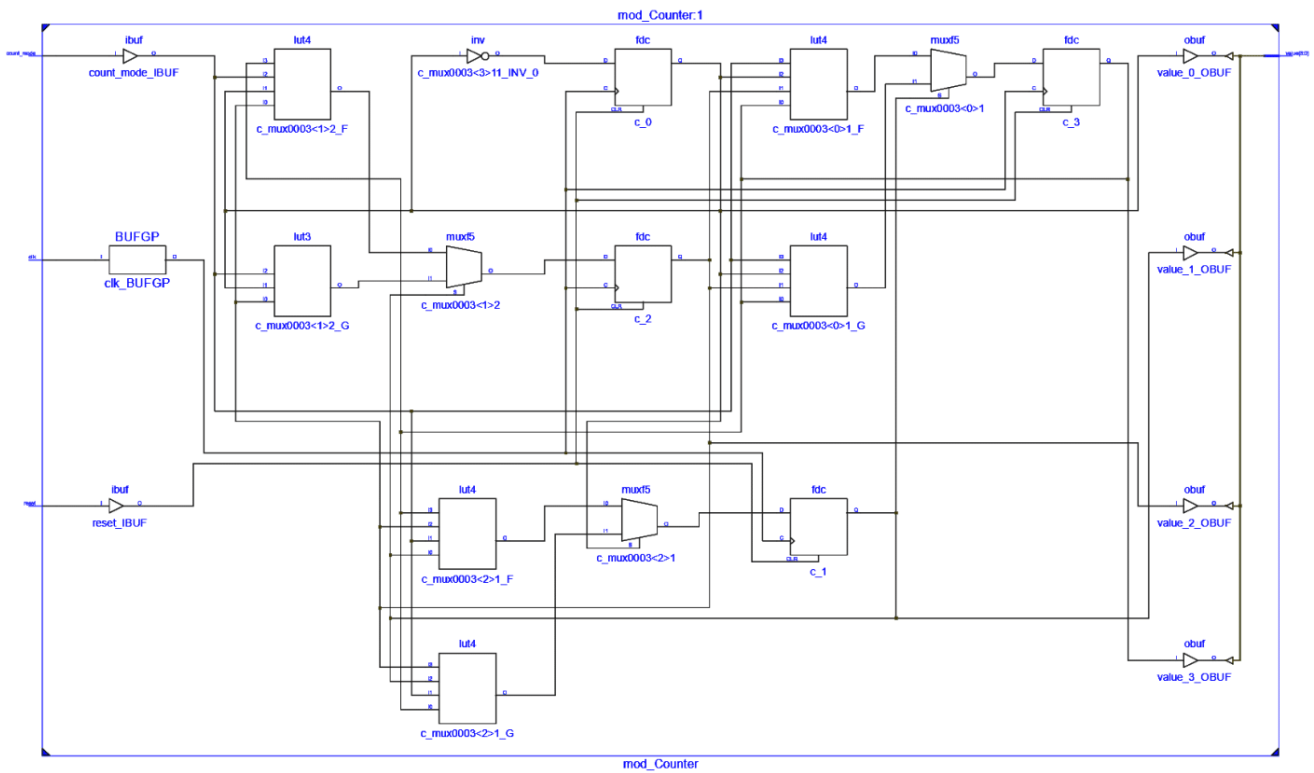


## Device Utilisation Summary:


Device Utilization Summary (estimated values)				[ - ]
Logic Utilization	Used	Available	Utilization	
Number of Slices	4	5888		0%
Number of Slice Flip Flops	4	11776		0%
Number of 4 input LUTs	7	11776		0%
Number of bonded IOBs	7	372		1%
Number of GCLKs	1	24		4%

## SPARTAN 6 SP-605

### RTL Schematic:

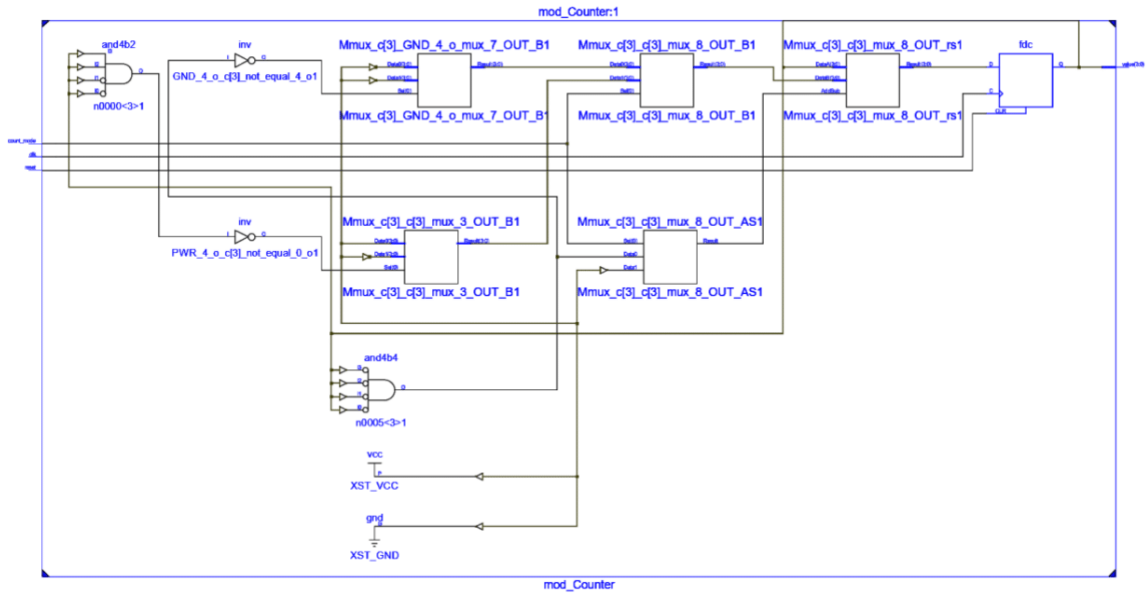

### Technology Schematic:

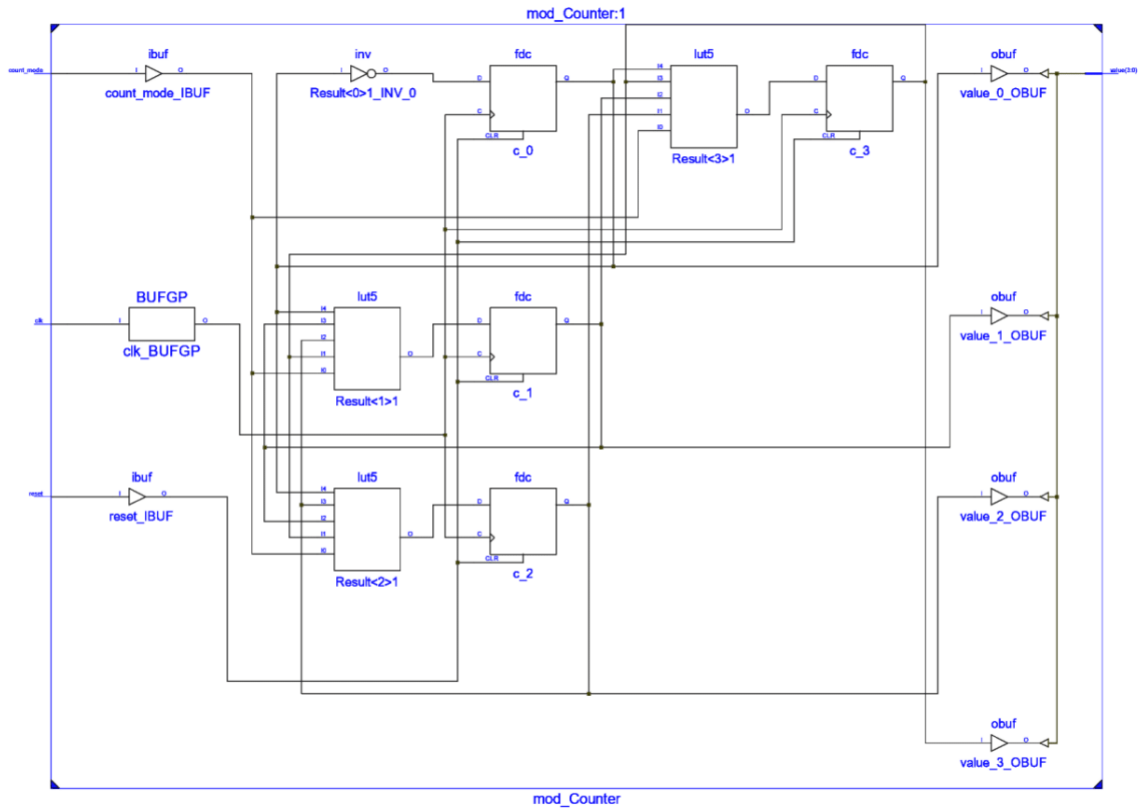

## Device Utilisation Summary:

Device Utilization Summary (estimated values)				<a href="#">[-]</a>
Logic Utilization	Used	Available	Utilization	
Number of Slice Registers	4	54576		0%
Number of Slice LUTs	4	27288		0%
Number of fully used LUT-FF pairs	0	8		0%
Number of bonded IOBs	7	296		2%
Number of BUFG/BUFGCTRLs	1	16		6%

## VHDL Test Bench:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_Counter IS
END tb_Counter;

ARCHITECTURE behavior OF tb_Counter IS
    COMPONENT mod_Counter
    PORT(
        clk           : IN  std_logic;
        reset         : IN  std_logic;
        count_mode: IN  std_logic;
        value          : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;

    signal clk           : std_logic := '0';
    signal reset         : std_logic := '0';
    signal mode          : std_logic := '0';
    signal value         : std_logic_vector(3 downto 0);

    constant clk_period : time := 75 ns;

BEGIN

    uut: mod_Counter PORT MAP (
        clk           => clk,
        reset         => reset,
        count_mode    => mode,
        value         => value
    );

    clk_process :process
```

```

begin
    clk <= '1';
    wait for clk_period/2;
    clk <= '0';
    wait for clk_period/2;
end process;

stim_proc: process
begin
    reset <= '1', '0' after 75ns;
    mode <= '1', '0' after 900ns;
    wait;
end process;
END;

```

### Simulation:



## Question 2

Design and simulate the behavioral model of a 4 bit shift register that can support the following modes of data transfer.

- Serial in parallel out (SIPO)
- Serial in serial out (SISO)
- Parallel in serial out (PISO)
- Parallel in parallel out (PIPO).

Use case statement for this design. Use one input `reg_mode` [`std_logic_vector` (1 downto 0)] to control the nature of behavior of the register. Use "00" for SIPO, "01" for SISO and so on.

**VHDL Module:**     *mod\_ShiftRegister.vhd*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mod_ShiftRegister is
    Port ( clk      : in  STD_LOGIC;
          reg_mode   : in  STD_LOGIC_VECTOR (1 downto 0);
          en         : in  STD_LOGIC;
          s_in       : in  STD_LOGIC;
          p_in       : in  STD_LOGIC_VECTOR (3 downto 0);
          s_out      : out STD_LOGIC;
          p_out      : out STD_LOGIC_VECTOR (3 downto 0));
end mod_ShiftRegister;

architecture Behavioral of mod_ShiftRegister is
    signal d : STD_LOGIC_VECTOR (3 downto 0) := "0000";

begin

    process(clk)
    begin
        if rising_edge(clk) then
            case reg_mode is
                when "00" =>
                    p_out(0) <= d(1); p_out(1) <= d(2);
                    p_out(2) <= d(3); p_out(3) <= s_in;
                    d(0) <= d(1); d(1) <= d(2);
                    d(2) <= d(3); d(3) <= s_in;
                    s_out <= '0';
                when "01" =>
                    s_out <= s_in;
                    p_out <= "0000";
            end case;
        end if;
    end process;

end Behavioral;
```




```

when "10" =>
    if en = '1' then d <= p_in;
    end if;
    s_out <= d(0);
    d(0) <= d(1); d(1) <= d(2);
    d(2) <= d(3); d(3) <= '0';
    p_out <= "0000";
when "11" =>
    p_out <= p_in;
    s_out <= '0';
when others =>
    end case;
end if;
end process;

end Behavioral;

```

### RTL Schematic:

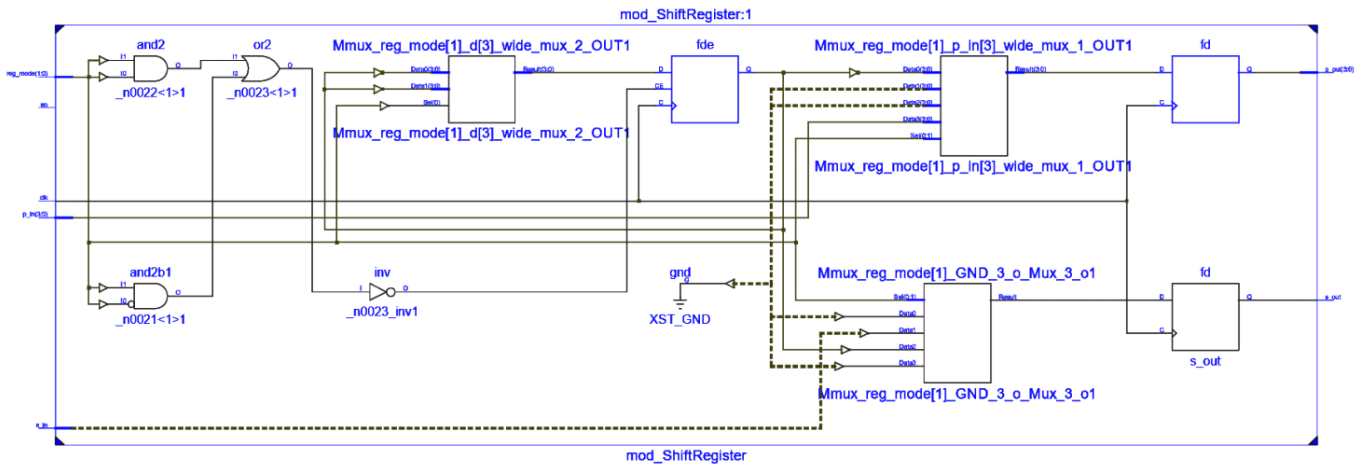

**VHDL Test Bench:**      *tb\_ShiftRegister.vhd*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_ShiftRegister IS
END tb_ShiftRegister;

ARCHITECTURE behavior OF tb_ShiftRegister IS
    COMPONENT mod_ShiftRegister
    PORT(
        clk           : IN  std_logic;
        reg_mode      : IN  std_logic_vector(1 downto 0);
        en            : IN  std_logic;
        s_in          : IN  std_logic;
        p_in          : IN  std_logic_vector(3 downto 0);
        s_out         : OUT std_logic;
        p_out         : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;

    signal clk           : std_logic := '0';
    signal reg_mode      : std_logic_vector(1 downto 0) := (others => '0');
    signal en           : std_logic := '0';
    signal s_in         : std_logic := '0';
    signal p_in         : std_logic_vector(3 downto 0) := (others => '0');

    signal s_out        : std_logic;
    signal p_out        : std_logic_vector(3 downto 0);

    constant clk_period : time := 100 ns;

BEGIN

    uut: mod_ShiftRegister PORT MAP (
        clk           => clk,
        reg_mode      => reg_mode,
        en            => en,
        s_in          => s_in,
        p_in          => p_in,
        s_out         => s_out,
        p_out         => p_out
    );

    clk_process :process
    begin
```

```

    clk <= '1';
    wait for clk_period/2;
    clk <= '0';
    wait for clk_period/2;
end process;


```

```

stim_proc: process
begin
    reg_mode <= "00", "01" after 400ns, "10" after 800ns, "11" after 1300ns;
    s_in <= '1', '0' after 100ns, '1' after 200ns, '0' after 400ns, '1' after
500ns, '0' after 800ns;
    en <= '0', '1' after 800ns, '0' after 900ns;
    p_in <= "0000", "0110" after 800ns, "1101" after 1300ns;
    wait;
end process;
END;

```

### Simulation:

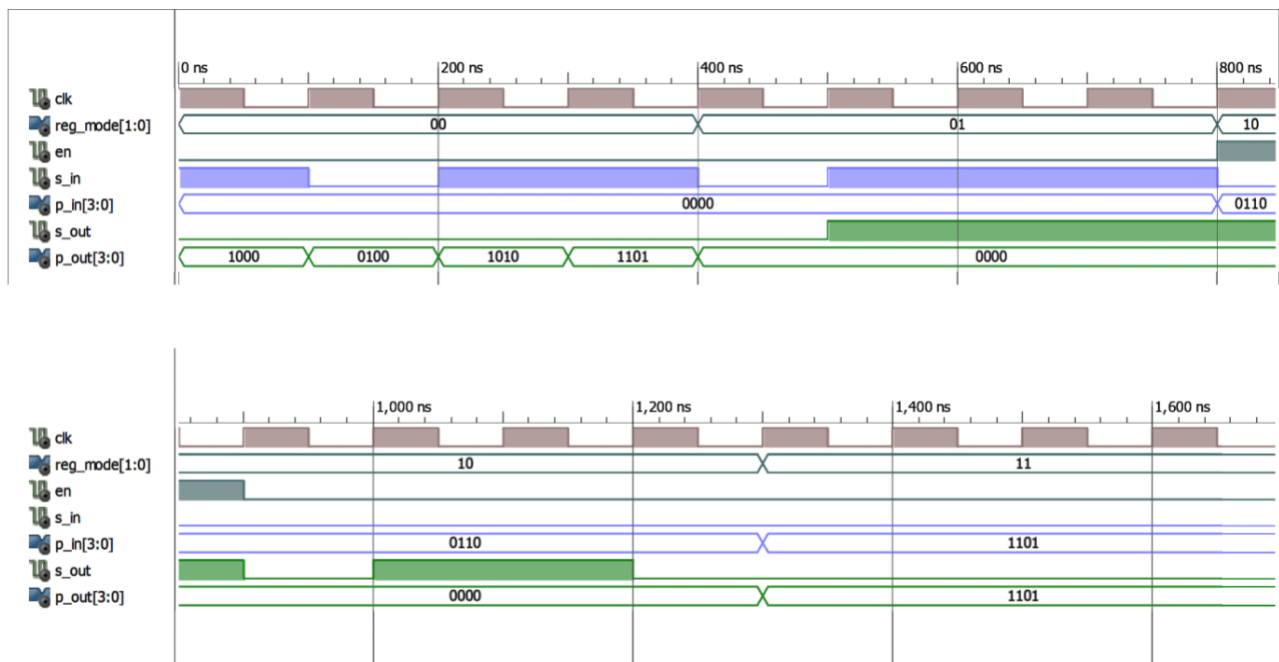

## Question 3

### Design the followings:

- Design and simulate the behavioral model of an 8 bit even parity generator.
- Design and simulate the behavioral model an 8 bit even parity checker.
- Design a top level module called parity and use the previously designed two modules as components to check whether the functionality of the two modules are in synchronization or not.

### VHDL Module:

#### mod\_genParity.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mod_genParity is
    Port ( d : in  STD_LOGIC_VECTOR (7 downto 0);
          p : out STD_LOGIC);
end mod_genParity;

architecture Behavioral of mod_genParity is

begin
    p <= d(0) xor d(1) xor d(2) xor d(3) xor d(4) xor d(5) xor d(6) xor d(7);
end Behavioral;
```

#### mod\_chkParity.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mod_chkParity is
    Port ( d : in  STD_LOGIC_VECTOR (7 downto 0);
          p : in  STD_LOGIC;
          o : out STD_LOGIC);
end mod_chkParity;

architecture Behavioral of mod_chkParity is

begin
    o <= not (d(0) xor d(1) xor d(2) xor d(3) xor d(4) xor d(5) xor d(6) xor d(7)
xor p);
end Behavioral;
```

### mod\_Parity.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mod_Parity is
    Port ( inp : in  STD_LOGIC_VECTOR (7 downto 0);
          oup : out STD_LOGIC);
end mod_Parity;


architecture Behavioral of mod_Parity is
    Component mod_genParity is
        Port ( d : in  STD_LOGIC_VECTOR (7 downto 0);
              p : out STD_LOGIC);
    end Component;

    Component mod_chkParity is
        Port ( d : in  STD_LOGIC_VECTOR (7 downto 0);
              p : in  STD_LOGIC;
              o : out STD_LOGIC);
    end Component;

    signal par : STD_LOGIC := '0';

begin
    GEN : mod_genParity port map (inp, par);
    CHK : mod_chkParity port map (inp, par, oup);
end Behavioral;
```

### RTL Schematic:

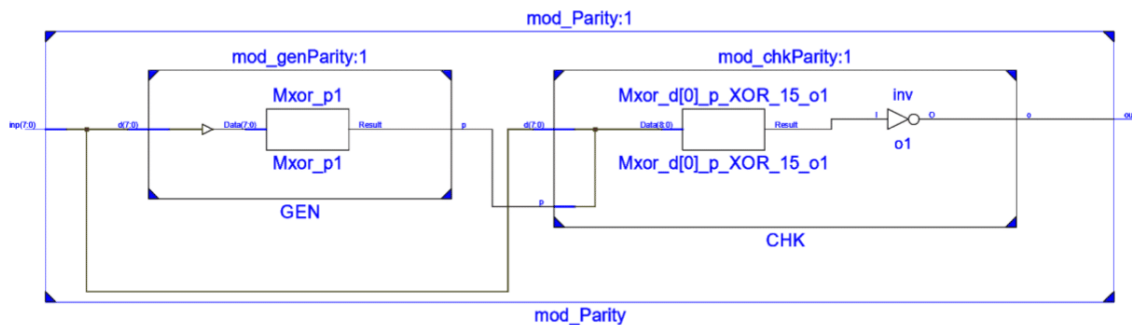

## VHDL Test Bench:

tb\_genParity.vhd


```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_genParity IS
END tb_genParity;

ARCHITECTURE behavior OF tb_genParity IS
    COMPONENT mod_genParity
    PORT(
        d : IN  std_logic_vector(7 downto 0);
        p : OUT std_logic
    );
    END COMPONENT;
    signal d : std_logic_vector(7 downto 0) := (others => '0');
    signal p : std_logic;

BEGIN
    uut: mod_genParity PORT MAP (
        d => d,
        p => p
    );
    stim_proc: process
    begin
        d <= "00000000";
        wait for 200ns;
        d <= "01001010";
        wait for 200ns;
        d <= "10001010";
        wait for 200ns;
        d <= "00110000";
        wait for 200ns;
        d <= "10110101";
        wait;
    end process;
END;
```

## Simulation:

 

tb\_chkParity.vhd


```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_chkParity IS
END tb_chkParity;

ARCHITECTURE behavior OF tb_chkParity IS
    COMPONENT mod_chkParity
    PORT(
        d : IN  std_logic_vector(7 downto 0);
        p : IN  std_logic;
        o : OUT std_logic
    );
    END COMPONENT;
    signal d : std_logic_vector(7 downto 0) := (others => '0');
    signal p : std_logic := '0';
    signal o : std_logic;

BEGIN
    uut: mod_chkParity PORT MAP (
        d => d,
        p => p,
        o => o
    );
    stim_proc: process
    begin
        d <= "00000000"; p <= '0';
        wait for 100ns; p <= '1';
        wait for 100ns;
        d <= "01001010"; p <= '0';
        wait for 100ns; p <= '1';
        wait for 100ns;
        d <= "10001010"; p <= '0';
        wait for 100ns; p <= '1';
        wait for 100ns;
        d <= "00110000"; p <= '0';
        wait for 100ns; p <= '1';
        wait for 100ns;
        d <= "10110101"; p <= '0';
        wait for 100ns; p <= '1';
        wait;
    end process;
END;
```

## Simulation:

 

### tb\_Parity.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_Parity IS
END tb_Parity;


ARCHITECTURE behavior OF tb_Parity IS
    COMPONENT mod_Parity
    PORT(
        inp : IN  std_logic_vector(7 downto 0);
        oup : OUT std_logic
    );
    END COMPONENT;
    signal inp : std_logic_vector(7 downto 0) := (others => '0');
    signal oup : std_logic;

BEGIN
    uut: mod_Parity PORT MAP (
        inp    => inp,
        oup    => oup
    );

    stim_proc: process
    begin
        inp <= "00000000";
        wait for 200ns;
        inp <= "01001010";
        wait for 200ns;
        inp <= "10001010";
        wait for 200ns;
        inp <= "00110000";
        wait for 200ns;
        inp <= "10110101";
        wait;
    end process;
END;
```




## Simulation:

 
 
## Question 4

Design a 8 bit barrel shifter. The circuit must shift the input vector of size 8 either 0 or 1 position to the left. When actually shifted (shift = 1), the LSB bit must be filled with '0'. If shift = 0, then  $out(i)=in(i)$ ; else, if shift = 1, then  $out(0)=0$  and  $out(i)=in(i-1)$ , for  $1 \leq i \leq 7$ . Write a concurrent code for this circuit and verify its behavior.



### VHDL Module:

modMux.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mod_mux is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          S : in  STD_LOGIC;
          O : out STD_LOGIC);
end mod_mux;

architecture Behavioral of mod_mux is

begin
    O <= A when S = '0' else B;
end Behavioral;
```

### mod\_BarrelShifter.vhd


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mod_BarrelShifter is
    Port ( shf : in  STD_LOGIC;
          inp : in  STD_LOGIC_VECTOR (7 downto 0);
          oup : out STD_LOGIC_VECTOR (7 downto 0));
end mod_BarrelShifter;

architecture Behavioral of mod_BarrelShifter is
    component mod_mux is
        Port ( A : in  STD_LOGIC;
              B : in  STD_LOGIC;
              S : in  STD_LOGIC;
              O : out STD_LOGIC);
    end component;

begin
    MUX0 : mod_mux port map ('0',    inp(0), shf, oup(0));
    MUX1 : mod_mux port map (inp(0), inp(1), shf, oup(1));
    MUX2 : mod_mux port map (inp(1), inp(2), shf, oup(2));
    MUX3 : mod_mux port map (inp(2), inp(3), shf, oup(3));
    MUX4 : mod_mux port map (inp(3), inp(4), shf, oup(4));
    MUX5 : mod_mux port map (inp(4), inp(5), shf, oup(5));
    MUX6 : mod_mux port map (inp(5), inp(6), shf, oup(6));
    MUX7 : mod_mux port map (inp(6), inp(7), shf, oup(7));
end Behavioral;
```

### Technology Schematic:

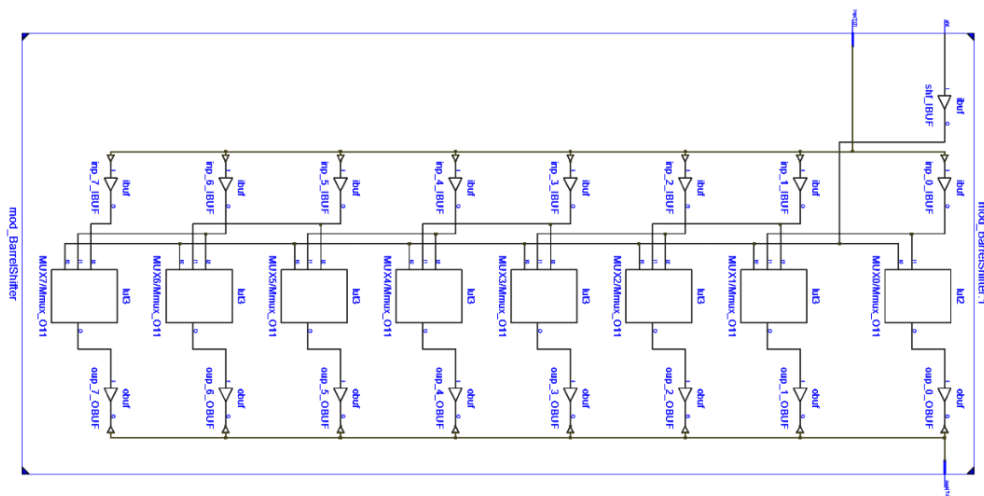

## VHDL Test Bench:      *tb\_mux.vhd*


```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_mux IS
END tb_mux;

ARCHITECTURE behavior OF tb_mux IS
    COMPONENT mod_mux
    PORT(
        A : IN  std_logic;
        B : IN  std_logic;
        S : IN  std_logic;
        O : OUT std_logic
    );
    END COMPONENT;
    signal A : std_logic := '0';
    signal B : std_logic := '0';
    signal S : std_logic := '0';
    signal O : std_logic;

BEGIN
    uut: mod_mux PORT MAP (
        A => A,
        B => B,
        S => S,
        O => O
    );
    stim_proc: process
    begin
        A <= '0', '1' after 500ns;
        B <= '0', '1' after 250ns, '0' after 500ns, '1' after 750ns;
        S <= '0', '1' after 250ns, '0' after 500ns, '1' after 750ns;
        wait;
    end process;
END;
```


## Simulation:

 

## Question 5

Design an 16 bit ALU (Arithmetic Logic Unit) as shown in the following figure and verify it's behavior with simulation

Unit	Function	Sel
Arithmetic	Transfer a	0000
	Increment a	0001
	Decrement a	0010
	Transfer b	0011
	Increment b	0100
	Decrement b	0101
	Add a and b	0110
	Add a and b with carry	0111
Logical	Complement a	1000
	Complement b	1001
	AND	1010
	OR	1011
	NAND	1100
	NOR	1101
	XOR	1110
	XNOR	1111

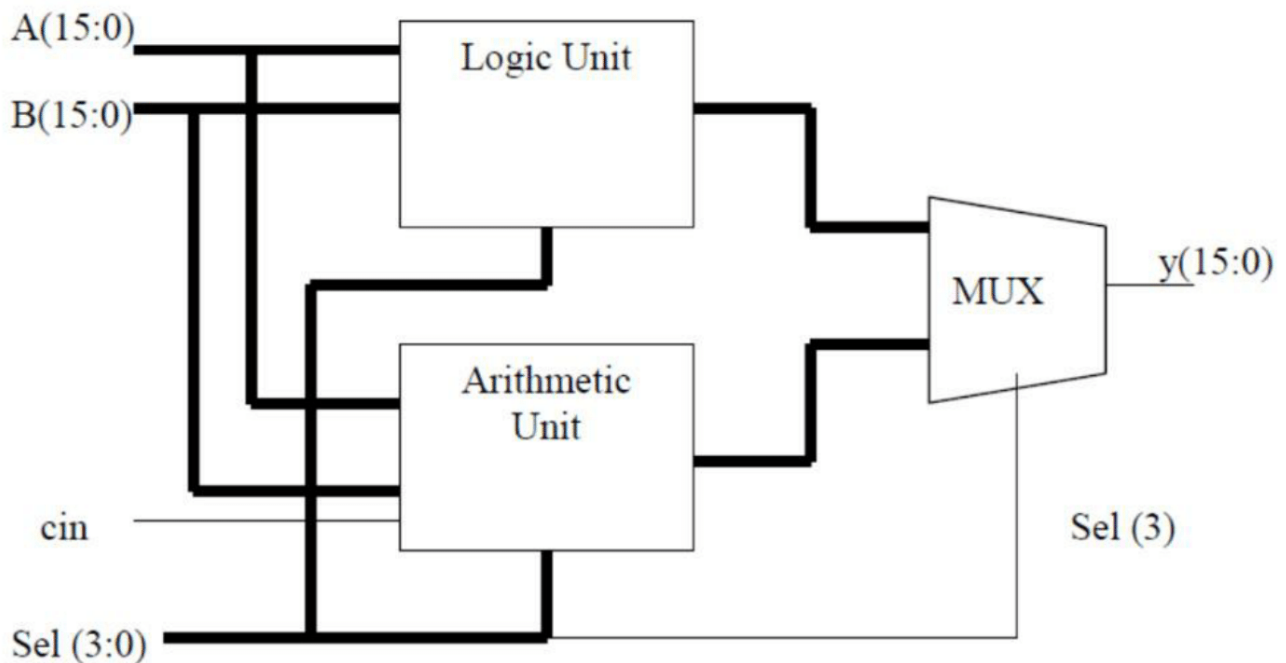

## VHDL Module:

arithUnit.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity arithUnit is
    Port ( S : in  STD_LOGIC_VECTOR ( 3 downto 0);
          A : in  STD_LOGIC_VECTOR (15 downto 0);
          B : in  STD_LOGIC_VECTOR (15 downto 0);
          C : in  STD_LOGIC;
          Y : inout STD_LOGIC_VECTOR (15 downto 0));
end arithUnit;

architecture Behavioral of arithUnit is
begin

process(S, A, B, C)
begin
    if(S(3) = '0') then
        case S is
            when "0000" => Y <= A;
            when "0001" =>
                Y <= STD_LOGIC_VECTOR(unsigned(A) + 1);
            when "0010" =>
                Y <= STD_LOGIC_VECTOR(unsigned(A) - 1);
            when "0011" => Y <= B;
            when "0100" =>
                Y <= STD_LOGIC_VECTOR(unsigned(B) + 1);
            when "0101" =>
                Y <= STD_LOGIC_VECTOR(unsigned(B) - 1);
            when "0110" =>
                Y <= STD_LOGIC_VECTOR(unsigned(A) + unsigned(B));
            when "0111" =>
                Y <= STD_LOGIC_VECTOR(unsigned(A) + unsigned(B));
                if(C = '1') then Y <= STD_LOGIC_VECTOR(unsigned(Y) + 1);
                end if;
            when others => Y <= "0000000000000000";
        end case;
    end if;
end process;

end Behavioral;
```

logicUnit.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity logicUnit is
    Port ( S : in      STD_LOGIC_VECTOR ( 3 downto 0);
          A : in      STD_LOGIC_VECTOR (15 downto 0);
          B : in      STD_LOGIC_VECTOR (15 downto 0);
          Y : inout    STD_LOGIC_VECTOR (15 downto 0));
end logicUnit;

architecture Behavioral of logicUnit is

begin

process(S, A, B)
begin
    if(S(3) = '1') then
        case S is
            when "1000" => Y <= not A;
            when "1001" => Y <= not B;
            when "1010" => Y <= A and  B;
            when "1011" => Y <= A or   B;
            when "1100" => Y <= A nand B;
            when "1101" => Y <= A nor  B;
            when "1110" => Y <= A xor  B;
            when "1111" => Y <= A xnor B;
            when others => Y <= "0000000000000000";
        end case;
    end if;
end process;

end Behavioral;
```

selMux.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity selMux is
    Port ( S : in  STD_LOGIC;
          P : in  STD_LOGIC_VECTOR (15 downto 0);
          Q : in  STD_LOGIC_VECTOR (15 downto 0);
          Y : out STD_LOGIC_VECTOR (15 downto 0));
end selMux;
```

architecture Behavioral of selMux is

begin

    Y <= P when S = '0' else Q;  
end Behavioral;

ALU.vhd

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity ALU is

    Port ( A : in   STD\_LOGIC\_VECTOR (15 downto 0);  
          B : in   STD\_LOGIC\_VECTOR (15 downto 0);  
          C : in   STD\_LOGIC;  
          S : in   STD\_LOGIC\_VECTOR ( 3 downto 0);  
          Y : out STD\_LOGIC\_VECTOR (15 downto 0));

end ALU;

architecture Structural of ALU is

    signal M, N, O : STD\_LOGIC\_VECTOR (15 downto 0);

begin

AU : entity work.arithUnit port map(S, A, B, C, M);


LU : entity work.logicUnit port map(S, A, B, N);

MX : entity work.selMux         port map(S(3), M, N, Y);

end Structural;



## RTL Schematic:

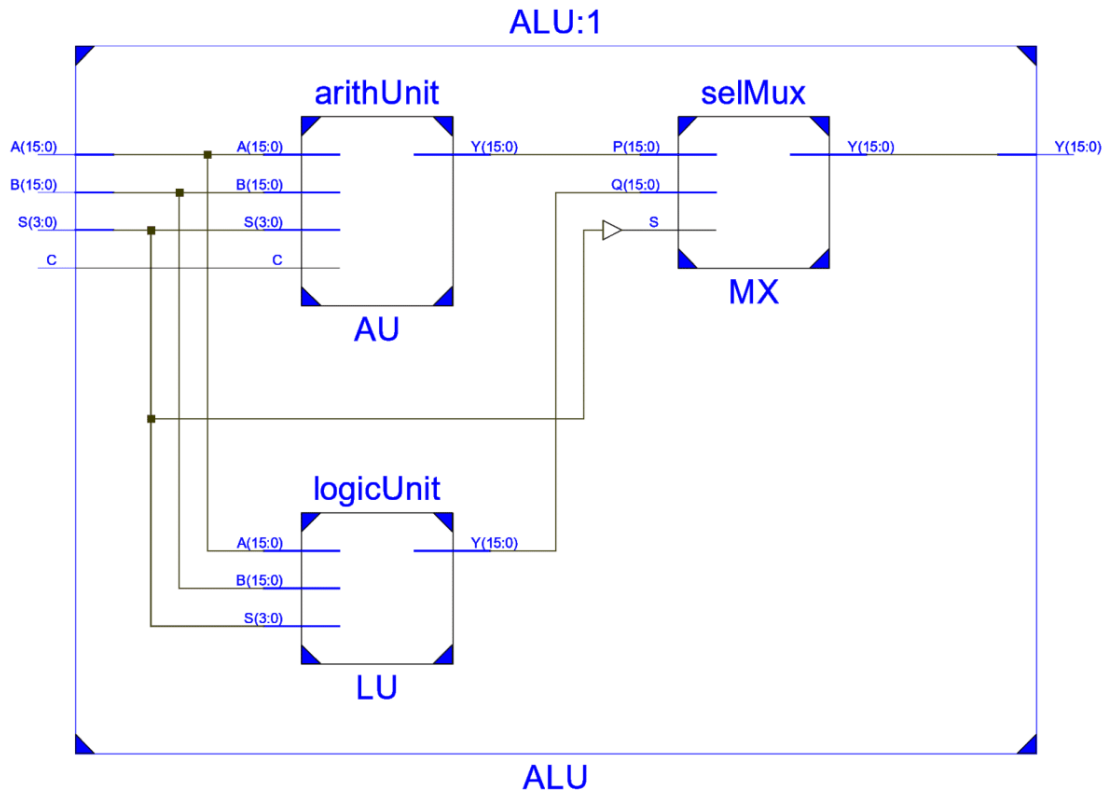

## VHDL Test Bench: *tb\_ALU.vhd*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY tb_ALU IS
END tb_ALU;

ARCHITECTURE behavior OF tb_ALU IS
    COMPONENT ALU
        PORT ( A : in  STD_LOGIC_VECTOR (15 downto 0);
              B : in  STD_LOGIC_VECTOR (15 downto 0);
              C : in  STD_LOGIC;
              S : in  STD_LOGIC_VECTOR ( 3 downto 0);
              Y : out STD_LOGIC_VECTOR (15 downto 0));
    END COMPONENT;

    SIGNAL a : STD_LOGIC_VECTOR (15 downto 0) := (others => '0');
    SIGNAL b : STD_LOGIC_VECTOR (15 downto 0) := (others => '0');
    SIGNAL c : STD_LOGIC := '0';
    SIGNAL s : STD_LOGIC_VECTOR ( 3 downto 0) := (others => '0');
```

```
SIGNAL y : STD_LOGIC_VECTOR (15 downto 0);
```

```
BEGIN
```

```
    uut: ALU PORT MAP(
```

```
        A => a,
```

```
        B => b,
```

```
        C => c,
```

```
        S => s,
```

```
        Y => y
```

```
    );
```

```
process
```

```
begin
```

```
    a <= "0101001010111010";
```

```
    b <= "1001001011011011";
```

```
    c <= '1';
```

```
    s <= "0000";
```

```
    while s >= "0000" loop
```

```
        wait for 100ns;
```

```
        s <= STD_LOGIC_VECTOR(unsigned(s) + 1);
```

```
    end loop;
```

```
    wait;
```

```
end process;
```

```
END;
```

### Simulation:

